

**ETL – Power Electronics  
T010**

**Thursday, 10/11/2016  
08:30 – 11:30**

WORKFORCE DEVELOPMENT AUTHORITY



P.O. BOX 2707 Kigali, Rwanda Tel: (+250) 255113365

---

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2016,  
TECHNICAL AND PROFESSIONAL STUDIES**

**EXAM TITLE: Power Electronics**

**OPTION: Electronics and Telecommunication (ETL)**

**DURATION: 3hours**

**INSTRUCTIONS:**

The paper is composed of **three (3) main Sections** as follows:

**Section I: Sixteen (16) compulsory questions. 55 marks**


**Section II: Attempt any three (3) out of five questions. 30 marks**

**Section III: Attempt any one (1) out of three questions. 15 marks**


**Note:**

***Every candidate is required to carefully comply with the above instructions. Penalty measures will be applied on their strict consideration.***

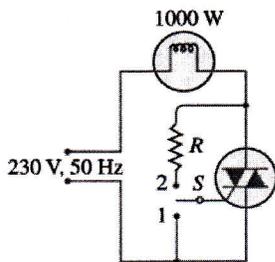- 01. Give the proper technical names of AC to DC, AC to AC, DC to AC, and DC to DC Converters? **4marks**
- 02. How a triac can be turned on? **2marks**
- 03. Explain the Silicon controlled rectifier (SCR)? **4marks**
- 04. An SCR can only control the positive half-cycle or negative half-cycle of a.c.  
**True or False** **2marks**
- 05. An SCR is a controlled unidirectional switch because it can conduct only in one direction.  
**True or False** **2marks**
- 06. Referring to figure below, explain the effect of triac when switch S is thrown to position 1 or 2. **5marks**




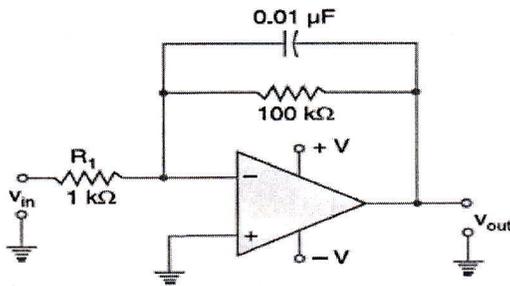- 07. The data sheet of a certain UJT gives  $\eta=0.6$ . Determine the peak-point emitter voltage  $V_p$  if  $V_{BB}=20V$  **3marks**
- 08. What are the Advantages of UJT? **3marks**
- 09. Write fully and correctly the sentence by filling in the following statements:  
A UJT has..... (two pn junctions; one pn junction; three pn junctions or none of the proposed components) **2marks**
- 10. A differential amplifier has an open-circuit voltage gain of 100. The input signals are 3.25 V and 3.15V. Determine the output voltage? **3marks**
- 11. Determine the lower frequency limit (critical frequency) for the integrator circuit shown in the following figure. **5marks**



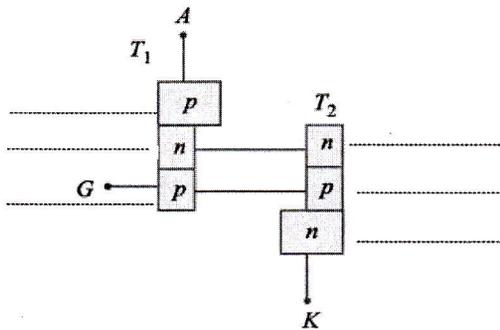- 12. Why not germanium controlled rectifier? **3marks**
- 13. Explain the two ways to turn on the silicon controlled rectifier? **5marks**
- 14. From the figure below, name all terminals? **6marks**

Fill out the names of corresponding terminals



15. What is holding current in SCR? 3marks

16. What value of capacitor is required to force commutate a thyristor with a turn-off time of  $20\mu\text{s}$  with a 96V battery and a full-load current of 100A? 3marks

**Section II. Choose and answer any three (3) questions.** 30marks

17. Differentiate:

- a) Thyristor from transistor. (List out seven points)
- b) Holding current from latching current.

10marks

18. a) Give the static characteristics of a DIAC.

- b) What are different methods used for controlling a TRIAC in normal operation? (Verify phase control and zero crossing detection)
- c) Differentiate the above stated methods.
- d) What are the mostly used quadrants of a TRIAC? Why?

10marks

19. A collector supply voltage  $V_{CC}=200\text{V}$ ,  $R_C=20\Omega$ ,  $t_{ON}=1.0\mu\text{s}$  and  $t_{OFF}=1.5\mu\text{s}$ . if the switching frequency is 5KHz, find: 10marks

- a) The turn-on energy loss
- b) The turn-off energy loss
- c) The switching power loss.

20. i) In a negative-feedback amplifier,  $A = 100$ ,  $\beta = 0.04$  and  $V_i = 50 \text{ mV}$ .

Find: (a) gain with feedback, (b) output voltage,  
(c) Feedback factor, (d) feedback voltage

ii) What are the five (5) applications of multivibrator? 10marks


21. List out five (5) disadvantages of load commutated chopper. 10marks

**Section III. Choose and answer any one (1) question.** 15marks


22. Answer to all of the following questions:

- a) Draw and explain why a Snubber circuit across the thyristor is necessary.

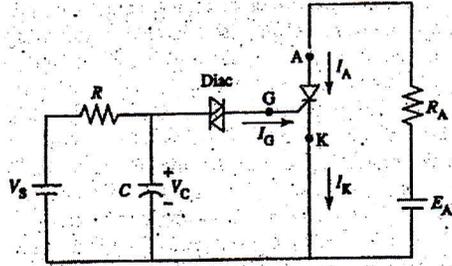- b) In the circuit bellow, explain how the SCR is triggered and propose one of the applications of the circuit.
- c) If the source  $E_A$  is replaced by an AC source, what would happen to the SCR after the DIAC turns off?
- e) If the source remains the same, DC source, what would happen if the DIAC turns off?
- f) What would happen if the capacitor become enables to produce a voltage greater or equal to the break over voltage of the DIAC?




23. Below is a circuit:

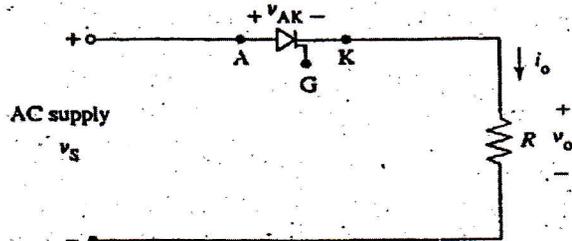

- i. Name it.
- ii. By the use of waveforms, draw the waveforms of the following electrical quantities across both SCR and LOAD on the same graph for the delay angle of  $30^\circ$  ( $\alpha = 30^\circ$ ).
  - a) Voltage
  - b) Current
- iii. Explain why the half wave rectifiers are not practically used.
- iv. Calculate the average output voltage for  $V_s = 120\text{v}$  and  $R = 10\text{k}$ .

24. Answer to all of the following questions:

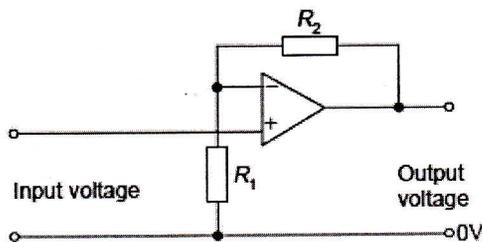- i) What are the main properties of an op- amp? (List out Three).
- ii) A differential amplifier has an open-loop voltage gain of 120 and a common input signal of 3.0 V to both terminals. An output signal of 24 mV results. Calculate the common-mode gain and the CMRR.
- iii) For the op amp shown in Figure below,  $R_1 = 4.7\text{ k}\Omega$  and  $R_2 = 10\text{ k}\Omega$ . If the input voltage is  $-0.4\text{ V}$ ,



Determine:

- (a) The voltage gain;
- (b) The output voltage