


**ELC - Electrotechnics**

**T001**

**Thursday, 23/11/2017**

**08:30 - 11:30 AM**

**WORKFORCE DEVELOPMENT AUTHORITY**

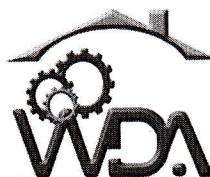

**P.O. BOX 2707 Kigali, Rwanda Tel: (+250) 255113365**

---

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2017,  
TECHNICAL AND PROFESSIONAL STUDIES**

**EXAM TITLE: ELECTROTECHNICS**

**OPTION: Electricity (ELC)**

**DURATION: 3 hours**

**INSTRUCTIONS:**

The paper is composed of the following sections:

**Section I: Eighteen (18) compulsory questions. 55 marks**


**Section II: Attempt any three (3) out of five questions. 30 marks**

**Section III: Attempt any one (1) out of three questions. 15 marks**

**Note:**

***Every candidate is required to carefully comply with the above instructions. Penalty measures will be applied on their strict consideration***

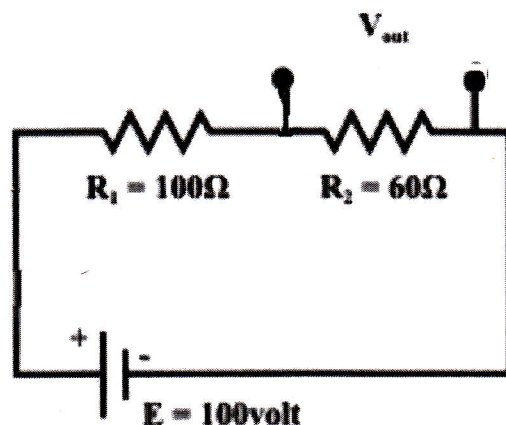01. For any two alternating signals, what do you understand by “leading signal”?  
**1 mark**
02. State the laws of electrostatics?  
**3 marks**
03. What do you understand by an over-excited synchronous motor?  
**2 marks**
04. A multiple plate capacitor has 10 plates, each of area 10 square cm and separation between 2 plates is 1 mm with air as dielectric. Determine the energy stored when voltage of 100 volts is applied across the capacitor.  
**3 marks**
05. Calculate the distribution factor for a 36 slots, 4-pole, single layer three-phase winding.  
**3 marks**
06. (a) Define the following expressions and mention their units: **3 marks**  
1) Self-inductance,  
2) Mutual inductance  
(b) Derive an expression for the energy stored in an inductor of self-inductance ‘L’ Henry carrying the current of ‘I’ amperes. **1 mark**
07. For the circuit shown in the figure below;




Calculate  $V_{out}$  across 60Ω resistor, ignoring the internal resistance of the source  $E$ . Use voltage division. **3 marks**

08. A 12-pole, 3-phase alternator driven at a speed of 500 r.p.m. supplies power to an 8-pole, 3-phase induction motor. If the slip of the motor, at full-load is 3%, calculate the full-load speed of the motor. **3 marks**

09. Express the difference between “linear” and “nonlinear” circuits?

**3 marks**

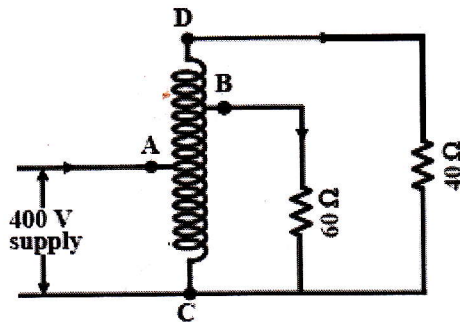10. An autotransformer has a coil with total number of turns  $N_{CD} = 200$  between terminals **C** and **D**. It has got one tapping at **A** such that the number of turns  $N_{AC} = 100$  and another tapping at **B** such that the number of turns  $N_{BA} = 50$ . As shown in figure.



Calculate the current and voltage for each resistance of the circuit, when 400 V supply is connected across AC. **4 marks**

11. Calculate the speed at which a 2-pole machine must rotate to obtain a voltage having frequency of 50Hz. **1 mark**

12. An alternating voltage  $e = 200 \sin 314t$  is applied to a device which offers an ohmic resistance of  $20 \Omega$  to the flow of current in one direction, while preventing the flow of current in opposite direction. Calculate for the current over one cycle:

- RMS value,
- average value and
- Form factor.

**3 marks**

13. Explain the following terms related to magnetic circuits:

- Reluctance
- Magnetomotive force

**2 marks**

14. What do you understand by the term ‘back e.m.f.’?

**1 mark**

15. A d.c. motor connected to a 460-V supply has an armature resistance of  $0.15 \Omega$ . Calculate:

- The value of back e.m.f. when the armature current is 120 A.
- The value of armature current when the back e.m.f. is 447.4V.

**4 marks**

16. A resistance of  $10\ \Omega$  is connected in series with two resistances each of  $15\ \Omega$  arranged in parallel. What resistance must be shunted across this parallel combination so that the total current taken shall be  $1.5\ \text{A}$  with  $20\ \text{V}$  applied? **5 marks**
17. A single-phase transformer has 400 primary and 1000 secondary turns. The net cross-sectional area of the core is  $60\ \text{cm}^2$ . If the primary winding be connected to a 50-Hz supply at  $520\ \text{V}$ , calculate:  
(i) The maximum value of flux density in the core.  
(ii) The voltage induced in the secondary winding. **4 marks**
18. Two batteries **A** and **B** are connected in parallel and load of  $10\ \Omega$  is connected across their terminals. **A** has an e.m.f. of  $12\ \text{V}$  and an internal resistance of  $2\ \Omega$ ; **B** has an e.m.f. of  $8\ \text{V}$  and an internal resistance of  $1\ \Omega$ . Use Kirchhoff's laws to determine:  
a) the values and directions of the currents flowing in each of the batteries;  
b) The value and direction of current in the external resistance.  
c) Also determine the potential difference across the external resistance. **6 marks**

**Section II. Choose and answer any three (3) questions only.**

**30 marks**

19. At  $25\ \text{Nm}$ , the armature current of the generator is  $16\ \text{A}$  at this value of torque. If the shunt field regulator is adjusted so that the flux is reduced by 15 per cent, the torque increases to  $35\ \text{Nm}$ . Determine the armature current at this new value of torque. **10 marks**
20. The power supplied to a three-phase induction motor is  $32\ \text{kW}$  and the stator losses are  $1200\ \text{W}$ . If the slip is 5 per cent, determine (a) the rotor copper loss, (b) the total mechanical power developed by the rotor, (c) the output power of the motor if friction and windage losses are  $750\ \text{W}$ , and (d) the efficiency of the motor, neglecting rotor iron loss. **10 marks**
21. A single phase a.c. generator supplies the following loads :  
(i) Lighting load of  $20\ \text{kW}$  at unity power factor;  
(ii) Induction motor load of  $100\ \text{kW}$  at p.f.  $0.707$  lagging;  
(iii) Synchronous motor load of  $50\ \text{kW}$  at p.f.  $0.9$  leading;  
Calculate the total kW and kVA delivered by the generator and the power factor at which it works. **10 marks**

22. An overhead 3-phase transmission line delivers 5000 kW at 22 kV at 0.8 p.f lagging. The resistance and reactance of each conductor is  $4 \Omega$  and  $6 \Omega$  respectively.

Determine:

- (i) Sending end voltage
- (ii) percentage regulation
- (iii) transmission efficiency.

**10marks**

23. A series motor runs at 800 rev/min when the voltage is 400V and the current is 25A. The armature resistance is  $0.4 \Omega$  and the series field resistance is  $0.2 \Omega$ . Determine the resistance to be connected in series to reduce the speed to 600 rev/min with the same current. **10 marks**


**Section III. Choose and answer any one (1) question.**

**15 marks**

- 24. a) State the Power Factor (PF)
- b) Describe the main factors of Power Factor that play an important role in AC circuits both **Intensity** and **Power dissipation** using formulae **of power in three phase AC circuit and Single phase Ac circuit**
- c) In case of Low Power Factor what will be happened?
- d) Describe the three causes of low Power factor
- e) How to improve PF?

**15 marks**

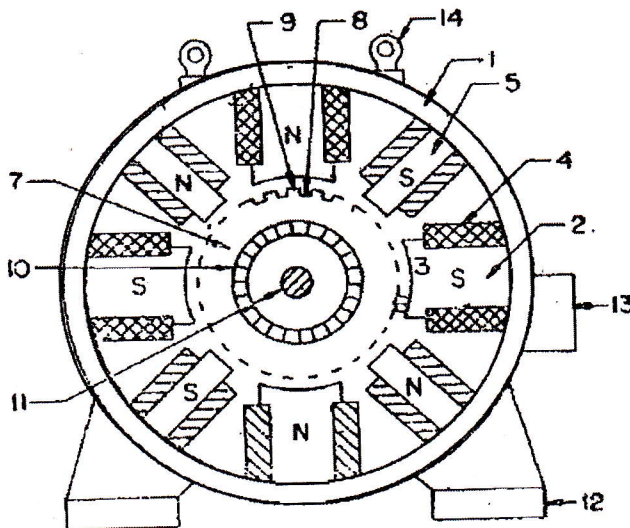25. With drawing, name the missing parts indicated by numbers on DC Machine.



**15 marks**

26. Initially a DC shunt motor shown on figure having  $r_a=0.5\Omega$  and  $R_f=220\Omega$  is running at 1000rpm drawing 20 A from 220 V supply. If the field resistance is increased by 5%. Calculate the new steady state armature current and speed of the motor. Assuming that the load torque to be constant.

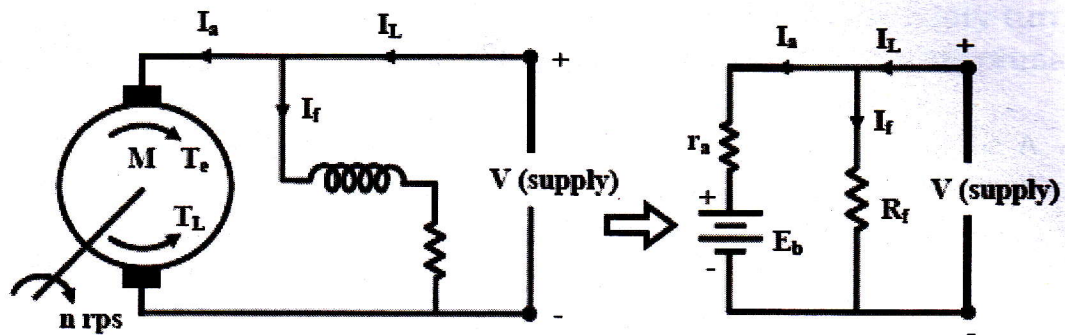


Figure : D.C shunt motor

15 marks

**Blank page**