


**CEL –Power Electronics and
Electromechanical Systems**

T009

Thursday, 23/11/2017

08:30 – 11:30 AM

WORKFORCE DEVELOPMENT AUTHORITY

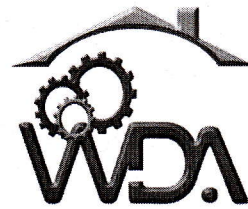

P.O. BOX 2707 Kigali, Rwanda Tel: (+250) 255113365

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2017,
TECHNICAL AND PROFESSIONAL STUDIES**

EXAM TITLE:

POWER ELECTRONICS AND ELECTROMECHANICAL SYSTEMS

OPTION: Computer Electronics (CEL)

DURATION: 3 hours

INSTRUCTIONS:

The paper is composed of **three (3) main Sections** as follows:

Section I: Fifteen (15) compulsory questions. 55 marks

Section II: Attempt any three (3) out of five questions. 30 marks


Section III: Attempt any one (1) out of three questions. 15 marks

Note:


Every candidate is required to carefully comply with the above instructions. Penalty measures will be applied on their strict consideration.

Section I. Fifteen (15) Compulsory questions**55 marks**

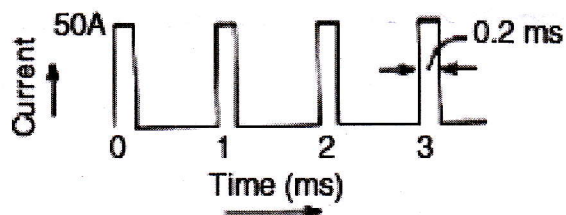- 01.** Explain the linear circuit elements in electrical circuit and give their examples. **3 marks**
- 02.** Define the following terms:
- a. Controllers
 - b. Sensors
 - c. Filters
 - d. Inverter
- 4 marks**
- 03.** Can an ordinary diode be used as a zener diode? Justify your answer. **3 marks**
- 04.** State the Current-voltage Switching classification. **4 marks**
- 05.** What are power converters that utilize natural commutation? **4 marks**
- 06.** The current waveform passing through a diode switch in a switch mode power supply application is shown in Figure below. Find the average, rms, and the peak current. **3 marks**



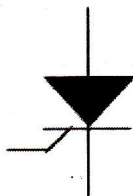- 07.** Which features must semiconductor possess in order to operate as an ideal switch? **5 marks**
- 08.** What are characteristics of The Practical Switch? **4 marks**
- 09.** What is the name of the semiconductor symbol shown below and put the names on its terminals **2 marks**



- 10.** List at least four Applications of uni-junction transistor (UJT). **4 marks**
- 11.** Classify choppers depending on the voltage output. **3 marks**

12. Which precautions that must be taken when triggering a Triac? **3 marks**
13. Explain the Thyristor commutation techniques. **5 marks**
14. What can happen if diodes are connected in:
 a. Series?
 b. Parallel? **4 marks**
15. Give at least four reasons which may cause the switching devices fail. **4 marks**

Section II. Choose and answer any three (3) questions. 30 marks


16. A Power MOSFET has $I_{DSS} = 2mA$, $R_{DS(ON)} = 0.3\Omega$, duty cycle $d = 50\%$, $I_D = 6A$, $V_{DS} = 100V$, $t_r = 100ns$ and $t_f = 200ns$. If the frequency of switching is 40 KHz, then find:
 i) on-state loss
 ii) off-state loss
 iii) turn-on switching loss
 iv) turn-off switching loss. **10 marks**
17. i) A power transistor has $V_{cc} = 208V$, $R_c = 20\Omega$,
 $V_{CE(SAT)} = 0.9V$; $V_{BE(SAT)} = 1.1V$ and $\beta = 10$
 Find :
 a) I_c ; I_B
 b) The power loss in collector (P_c).
 c) Power loss in base (P_B)
 ii) Draw construction of SCR using two transistor models. **10 marks**
18. What is IGBT? Draw the switching characteristics of IGBT. **10 marks**
19. The BJT is specified to have a range of 8 to 40. the load resistance in $R_e = 11\Omega$. The DC supply voltage is $V_{cc} = 200V$ and input voltage to the base circuit is $V_B = 10V$. if $V_{CE(SAT)} = 1.0V$ and $V_{BE(SAT)} = 1.5V$.

Find :

- a) The value of R_B that results in saturation with a overdrive factor of 5.
- b) The forced β_f .
- c) The power loss P_T in the transistor.

10 marks

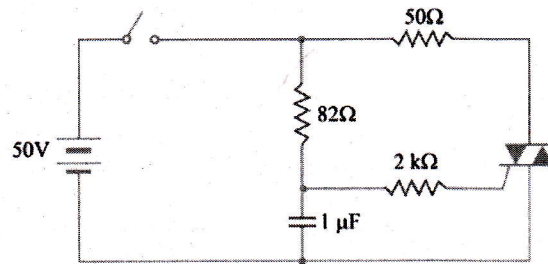20. a) In figure below, the switch is closed. if the triac has fired, what is the current through 50Ω resistor when:
- i) Triac is ideal
 - ii) Triac has a drop of 1V



- b) A d.c. to d.c. chopper operates from a 48 V battery source into a resistive load of 24Ω . The frequency of the chopper is set to 250Hz. Determine the average and rms load current and load power values when chopper on-time is 1ms.

10 marks

Section III. Choose and answer any one (1) question.

15 marks

21. Briefly, explain the Modes of Operation in silicon controlled rectifier (SCR).
22. A separately excited DC motor has the following parameters: 220V, 100A and 1450 rpm. Its armature has a resistance of 0.1Ω . In addition, it is supplied from a 3 phase fully-controlled converter connected to a 3-phase AC source with a frequency of 50 Hz and inductive reactance of 0.5Ω and 50Hz. At transport factor $(\alpha) = 0$, the motor operation is at rated torque and speed. Assume the motor brakes re-generatively using the reverse direction at its rated speed. Calculate the maximum current under which commutation is not affected.
23. Explain the formation of a potential barrier in a p-n junction of a semiconductor.