

*[Signature]*  
ETL - Power Electronics

**T078**

**Thursday, 31/10/2013**

**8:30 –11:30 AM**

WORKFORCE DEVELOPMENT AUTHORITY



P.O.BOX 2707 Kigali, Rwanda Tel: (+250) 255113365

---

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2013;**  
**TECHNICAL AND PROFESSIONAL TRADES**

**EXAM TITLE:** Power Electronics

**OPTION:** Electronics and Telecommunication (ETL)

**DURATION:** 3hours

**INSTRUCTIONS:**

The paper is contains Three **(2)** Sections:

Section I: Sixteen **(16)** questions, all **Compulsory.** **55marks**

Section II: Five **(5)** questions, **Choose any Three (3).** **30marks**

Section III: Two **(2)** questions, **Choose any One (1).** **15marks**

## **Section I: All the 16 questions are Compulsory      55marks**

01. Explain why is IGBT a voltage controlled device.      1mark
02. A voltmeter shows 230 VAC. What does it mean?      1mark
03. What are the different types of power MOSFET?      2marks
04. Differentiate latching current from holding current in case of a thyristor.      2marks
05. What are the main components used for isolating the Power Circuits, Power Semiconductor from the low-power circuit?      2marks
06. Describe a snubber circuit and precise its function.      2marks
07. What are the different types of chopper with respect to commutation process?      3marks
08. Differentiate the structure of a DIAC from that of a bipolar Transistor.      3marks
09. What are the different methods of firing circuits for line commutated converter?      3marks
10. How is the inverter circuit classified based on commutation circuitry?      4marks
11. Identify different losses that occur in a thyristor during working conditions.      4marks
12. Identify five (5) among different applications of controlled rectifier.      5marks
13. Describe a dc chopper and identify its main characteristics.      5marks
14. What is the difference between power diode and signal diode?      6marks
15. Identify in the following components which are current driven and those which are voltage driven: SCR; GTO; GTR; MCT; IGCT; SIT.      6marks
16. Explain why GTOs are more used in power converters compared to SCRs.      6marks


## **Section II. Choose and Answer any three questions.    30marks**

17. A UJT has 10V between its bases and is characterized by intrinsic stand-off ratio of 0.6; inter-base resistance of  $10\text{k}\Omega$ . The forward voltage drop in the pn junction is 0.7V. Determine the value of  $R_{B1}$  and  $R_{B2}$ ; the standoff voltage and the peak-point voltage.      10marks
18. An operational amplifier has feedback resistor  $R_f = 12\text{K }\Omega$  and the resistances in the input sides are  $R_1=12\text{K }\Omega$ ,  $R_2=2\text{K }\Omega$  and  $R_3=3\text{K }\Omega$  with the corresponding inputs voltages applied on inverting terminal  $V_{i_1} = +9\text{V}$ ,  $V_{i_2} = -3\text{V}$  and  $V_{i_3} = -1\text{V}$ . Non-inverting terminal is grounded. Calculate the output voltage.      10marks


- ~~Q~~ 19. Identify different types of filters commonly used in power supply circuits and give corresponding schematics. **10marks**
- (8) 20. a) Draw the circuit diagram of Four-diode Full-wave Bridge Rectifier and show the direction of the current through different diodes. **4marks**
- b) Identify its advantages and disadvantages. **6marks**
21. Draw the circuit of an OPAMP non-inverting voltage feedback amplifier and deduce the equation for its closed-loop gain. **10marks**
- (9)

### Section III. Choose and answer any One (1) question **15marks**

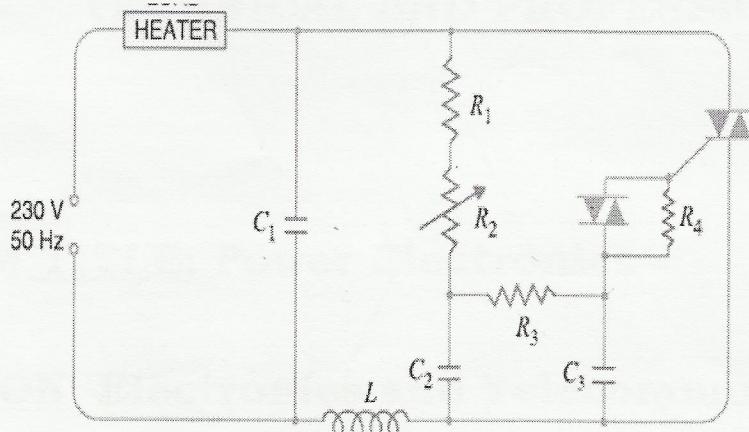22. Describe the behavior the following circuit : **15marks**



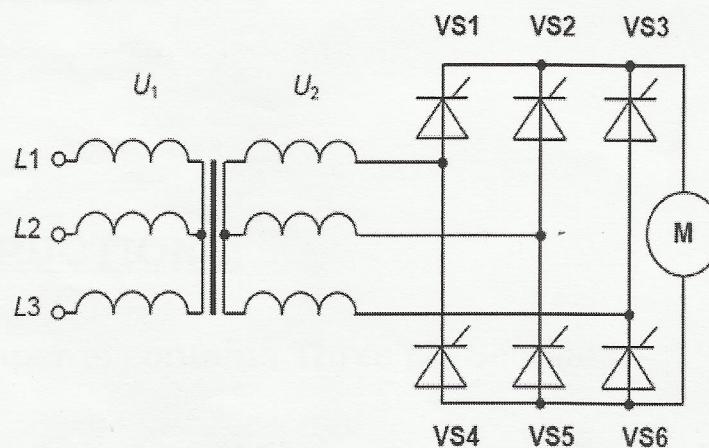23. Analyze the circuit represented bellow and answer to the questions :



- a) What is the type of that circuit? **1mark**
- b) Identify its main characteristics. **6marks**
- c) Determine the switching order of the elements represented by VS1,VS2,...,VS6. **6marks**
- d) What will happen if the element M possesses high inductance? **2marks**

## SECTION I.

Do not  
write in  
this margin

Q1. IGBT is voltage controlled because :

- the controlling parameter is gate-emitter voltage. 1
- the gate terminal is insulated. 1 *Consider one only*
- the output current is controlled by input voltage. 1

1mark

Q2. 230 VAC shown by voltmeter means that :

- It is the rms (root mean square) value. 1 *Consider one only* 1marks
- or - It is the effective value of AC voltage. 1

80

Q3. Types of power MOSFET

N-channel MOSFET 1

- Enhancement Only MOSFET  $\swarrow$  P-channel MOSFET 1 *Consider two*.

2marks

- Depletion-Enhancement only MOSFET  $\swarrow$  P-channel MOSFET 1

Q4. - Latching current is the minimum value of anode current which it must attain during turn on process to maintain conduction when gate signal is removed. 1

2marks

- The Holding current is defined as the minimum value of anode current below which it must fall to for turning off the thyristor. 1 *Consider two only*

- Holding current is the maximum anode current, gate being open, at which SCR is turned-off from on condition. 1

Q5. Components used isolating power circuits :


- opto-couplers (like Opto-triac, Opto-thyristor, Relays) *Consider two only*

2marks

- transformers 1 *Consider two only*

- Solid state relay 1

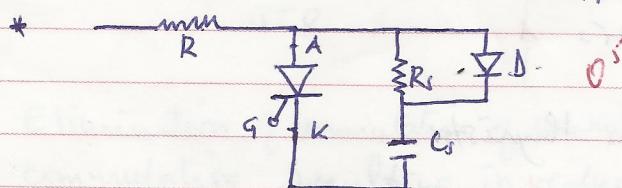Q6. Snubber circuit and its application :



2marks

\* It consists of a series combination of a resistor and a capacitor in parallel with the thyristors. 0.5


\* It is mainly used for  $\frac{dv}{dt}$  protection. 1

07. Types of chopper w.r.t. to commutation process.


- Voltage commutated chopper 1
- current commutated chopper 1
- Load commutated chopper 1 Consider three only
- Line commutated chopper 1 Review notes
- Forced commutated chopper 1 In terms of turn-off

Do not write in  
this margin

08. DIAC structure

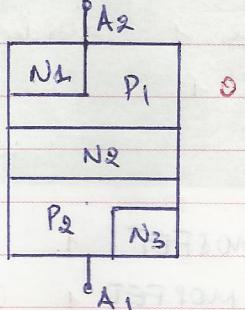

Bipolar transistor:

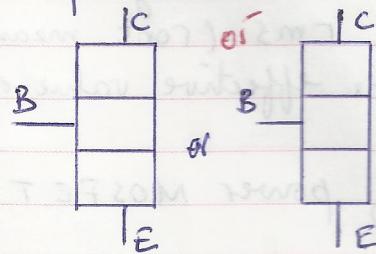

3marks

- It has four junctions 01
- It has two terminals 01
- There is no terminal attached to base 01
- Three regions are identical <sup>layer</sup> nearly insite 01
- The doping concentration are identical 01  
to give the device symmetrical properties.

- It has three junctions 01
- It has three terminals 01
- All terminals are attached to 01
- The regions are not identical <sup>base</sup> 01  
Observe only three  
consider

09. Methods of firing circuits for line commutated converter :

- UJT firing circuit 1
- The cosine wave crossing pulse timing control 1
- Digital firing schemes - 1

3marks

10. Classification of inverters based on commutation circuitry :

- Line commutated inverters 1
- load commutated inverters 1
- Self-commutated inverters 1
- Forced commutated inverters 1

4marks

11. Different losses occurring in thyristor :

- Forward conduction losses 1
- Loss due to leakage current during forward and reverse blocking 1
- Switching losses at turn-on and turn-off 1
- Gate triggering loss. 1

4marks

12. Five applications of controlled Rectifier.
- Steel rolling mills, printing process, textile mills (different machines) employing DC motor drives 1
  - DC traction 1
  - Electro-chemical and electro-metallurgical process 1
  - Portable hand tool drives 1
  - Magnet power supplies 1 consider five only.
  - HVDC transmission system. 1
  - Rectification 1

Do not write in this margin

5 marks.

13. \* A DC chopper is a high speed static switch used to obtain variable DC voltage from a constant DC voltage. 1

DC chopper characteristics :

- \* High efficiency 1
- \* Smooth acceleration 1
- \* Fast dynamic response 1
- \* Regeneration 1

5 marks.

14. Difference between power diode and signal diode.

Power diode

- Constructed with n-layer, called drift region between p+ layer and n+ layer 1
- The voltage, current and power ratings are higher 1.
- Power diodes operate at high speeds 1
- lower switching speed

signal diode

- Drift region is not present 1
- Voltage, current, and power are lower 1
- Operate at higher switching speed 1
- Operate at low speed

6 marks.

15. Current driven devices

SCR 1

GTO 1

GTR 1

Voltage controlled devices.

MCT 1

IGCT 1

SIT 1

6 marks.

16. a) Elimination of commutation of commutating components in forced commutation resulting in reduction in cost, weight and volume,
- b) Reduction in acoustic noise and electromagnetic noise due to elimination of commutation chokes 1
- c) Faster turn-off, permitting high switching frequencies 1
- d) Improved efficiency of the converters 1

6 marks.

## SECTION II.

Do not  
write in  
this margin

17. a) Determine the value of  $R_{B1}$  and  $R_{B2}$ .

$$V_{BB} = 10V, \eta = 0.6, R_{BB} = 10k\Omega, V_D = 0.7V$$

$$R_{BB} = R_{B1} + R_{B2} \quad 1$$

$$10 = R_{B1} + R_{B2} \quad 1$$

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}} \quad 1$$

$$0.6 = \frac{R_{B1}}{10} \quad 1$$

6 marks

$$R_{B1} = 0.6 \times 10k\Omega = 6k\Omega \quad 1$$

$$R_{B2} = 10 - R_{B1} = 10 - 6 = 4k\Omega \quad 1$$

10 marks

- b) Standoff voltage

$$V_{\text{standoff}} = \eta \times V_{BB} \quad 1$$

$$= 0.6 \times 10 = 6V \quad 1$$


2 marks

- c) Peak-point voltage

$$V_{\text{peak-point}} = n \times V_{BB} + V_D \quad 1$$

$$= 6 + 0.7 = 6.7V \quad 1$$

2 marks

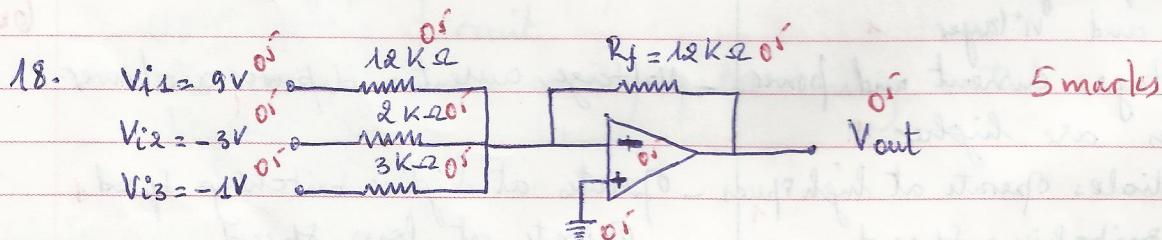

5 marks

10 marks

$$V_{\text{out}} = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right) \quad 1$$

$$= - \left( \frac{12}{12} (9) + \frac{12}{6} (-3) + \frac{12}{3} (-1) \right) \quad 1$$

$$= - (9 - 18 - 4) \quad 1$$


$$= - 9 + 18 + 4 \quad 1$$

$$= 13V \quad 1$$


# 19. Types of filters.

Do not  
write in  
this margin


(i) capacitor : C filter 1

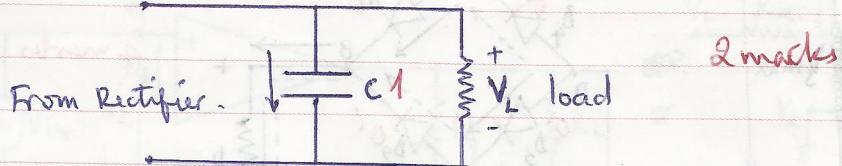


(ii) Series inductor filter : L filter 1

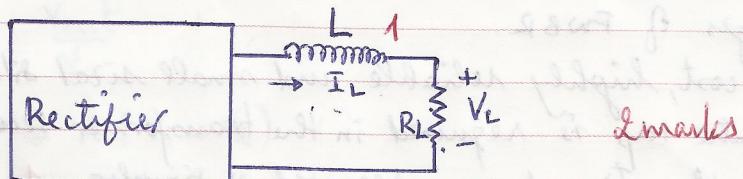


(iii) choke input filter : LC filter 1

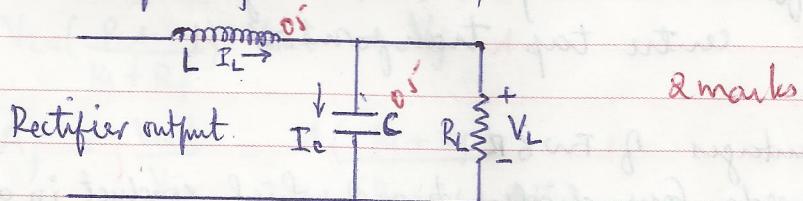

(iv)  $\Pi$  Filter : CLC filter 0's

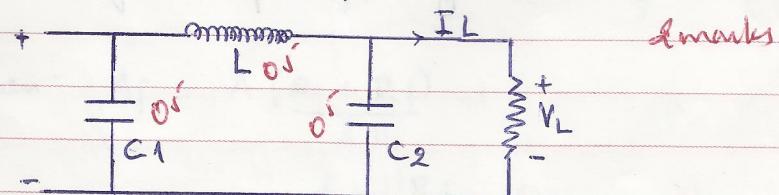


(v) RC filter 0's

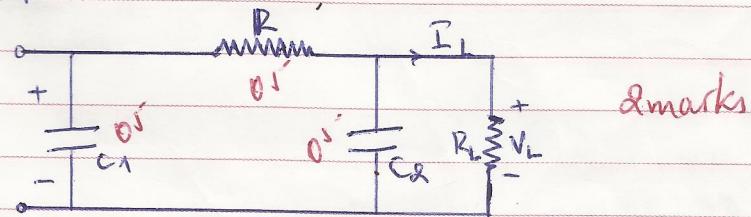

Ques. a) Four diode full wave bridge rectifier. (FWBR)

Do not  
write in  
this margin

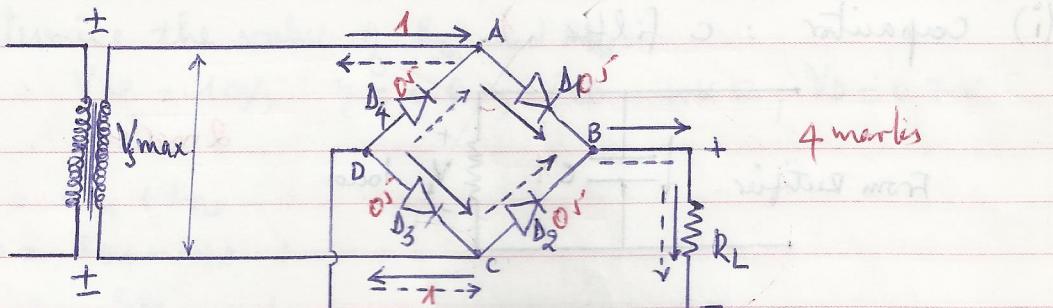

b) \* Advantages of FWBR.

1. low cost, highly reliable and small sized silicon diodes 1
2. No centre tap is required in the transformer secondary; the transformer required is simpler. 1
3. The PIV is one half that of centre-tap rectifier 1
4. Transformer Utilization factor (TUF) is higher than that of centre tap transformer. 1

10 marks

4 marks

\* Disadvantages of FWBR.


1. It needs four diodes, two of which conduct in alternate half cycles
2. Total Voltage drop in diodes becomes double of that in case of centre tap rectifiers. 1

2 mark

# 21. OP-AMP non-inverting Voltage feedback amplifier.

Do not  
write in  
this margin

Schematic diagram.

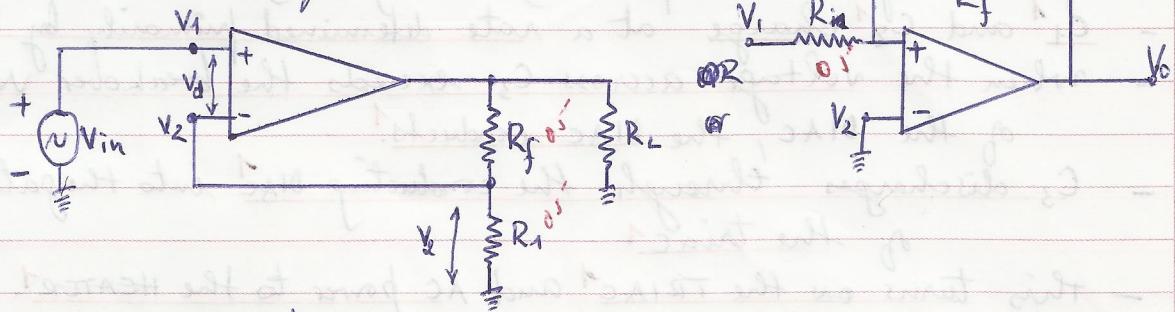

$$A_f = \frac{V_{out}}{V_{in}} \quad 1$$

$$V_{out} = A(V_1 - V_2) \quad 1$$

$$V_1 = V_{in} \quad 1$$

$$V_2 = \left( \frac{R_1}{R_1 + R_f} \right) V_{out} = V_f \quad 1$$

$$A_f = \frac{V_{out}}{V_{in}} = A \left( \frac{R_1 + R_f}{R_1 + R_f + A R_1} \right) \quad 1$$

As  $A R_1 \gg (R_1 + R_f)$  and  $R_1 + R_f + A R_1 \approx A R_1$  2

$$\begin{aligned} \text{Then } A_f &= A \left( \frac{R_1 + R_f}{A R_1} \right) \quad 1 \\ &= 1 + \frac{R_f}{R_1} \quad 1 \end{aligned}$$

### SECTION III.

Do not  
write in  
this margin

22. - Input voltage increase positively<sup>1</sup> or negatively<sup>1</sup>
- $C_1$ <sup>1</sup> and  $C_2$ <sup>1</sup> charge at a rate determined primarily by  $R_2$ <sup>1</sup>
  - when the voltage across  $C_3$  exceeds the breakdown voltage<sup>1</sup> of the DIAC, the DIAC conducts.<sup>1</sup>
  - $C_3$  discharges through the conducting DIAC into the gate of the triac<sup>1</sup> 15 mark
  - this turns on the TRIAC<sup>1</sup> and AC power to the HEATER<sup>1</sup>.
  - By adjusting the value of  $R_2$ <sup>1</sup>, any portion of positive or negative half cycles of ~~and~~ supply voltage can be passed through the heater.<sup>1</sup>
  - this permits a smooth control<sup>1</sup> of the heat output from heater.<sup>1</sup>

23. a) It is a three-phase bridge rectifier using 6 thyristors<sup>1</sup> or it is a 3φ controlled bridge rectifier.
- b) 1 - This circuit does not require neutral line of the 3-phases<sup>1</sup>
- 2 - It is a 2 quadrant rectifier.<sup>1</sup>
- 3 - There is more than one open thyristor in cathode group or anode group.<sup>1</sup>
- 4 - Voltage ripple is low because the output voltage consists of 6 pulses per period<sup>2</sup> 15 marks
- 5 - At least one thyristor from each group must conduct to facilitate the flow of the motor current<sup>1</sup>
- 6 - Determine the switching order of the elements represented

c) The switching order :

- 1)  $V_{S1} + V_{S6}$  1
- 2)  $V_{S6} + V_{S2}$  1
- 3)  $V_{S2} + V_{S4}$  1
- 4)  $V_{S4} + V_{S3}$  1
- 5)  $V_{S3} + V_{S5}$  1
- 6)  $V_{S5} + V_{S1}$  1

d) If the element M (which constitutes a load to the circuit: for example a motor) possesses high inductance, the forward current continues to flow on the negative anode voltage<sup>1</sup> and the switching-off of the thyristor is delayed.<sup>1</sup>