

CEL&ETL - Analog and Digital
Systems

T005

Friday, 13/11/2015

14:00 - 17:00

WORKFORCE DEVELOPMENT AUTHORITY



P.O. BOX 2707 Kigali, Rwanda Tel: (+250) 255113365

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2015,
TECHNICAL AND PROFESSIONAL TRADES**

EXAM TITLE: Analog and Digital Systems

OPTIONS: - Computer Electronics (CEL)

- Electronics and Telecommunication ETL)

DURATION: 3hours

INSTRUCTIONS:

The paper is composed of **three (3) Sections:**

Section I: Fifteen (15) questions, all **Compulsory**.

55marks

Section II: Five (5) questions, **Choose Three (3) only**.

30marks

Section III: Three (3) questions, **Choose only One (1)**.

15marks

Every candidate is required to strictly obey the above instructions. Punishment measures will be applied to anyone who ignores these instructions.

Section I. Fifteen (15) Compulsory questions.

55marks

01. What are the names of three terminals from the figure 1?

2marks

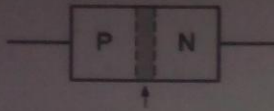


Figure 1

02. Divide 11011_2 by 100_2

4marks

03. Distinguish the four systems of arithmetic which are often used in digital circuits.

4marks

04. Give the principal three types of multivibrators.

3marks

05. Find the Boolean expression for the output of figure 2 and compute its value when $A = B = C = 1$ and $X = 0$

5marks

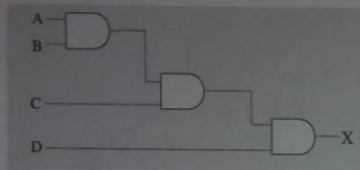


Figure 2

06. What are the three important classes of devices used to build digital electronic systems?

3marks

07. List out the two broad categories of logic devices.

2marks

08. Give the composition of a programmable logic array (PLA) device.

3marks

09. Identify the two types of counters.

4marks

10. Based on the method used to load data onto and read data from shift registers, classify them.

6marks

11. Determine the number of flip-flops required to construct:

- i. a MOD-10 ring counter,
- ii. a MOD-10 Johnson counter.

6marks

12. Draw a binary ladder network as the most widely used network for digital-to-analogue conversion.

4marks

13. List the types of D/A Converters.

3marks

14. Define a microprocessor.

2marks

15. Depending upon the nature of the memory cell used, there are two types of RAM, what are them.

4marks

Section II. Answer any three (3) questions of your choice

(Do not choose more than three questions).

30marks

16. i) A shunt motor runs 500r.p.m on a 200V circuit. Its in armature resistance is 0.5Ω and the current taken is 30A in addition to field current. What resistance must be placed in series in order that the speed may be reduced to 300r.p.m? The current in armature remains the same.


ii) A 500V shunt motor runs at its normal speed of 250r.p.m when the armature current is 200A. The resistance of armature is 0.12Ω .

Calculate the speed when a resistance is inserted in the field reducing the shunt field to 80% of normal value, and the armature current is 100A. **10marks**

17. a) Define rectification.
 b) Design a half wave voltage rectifier circuit.
 c) From the circuit you designed in (b) calculate V_{DC} .
 d) How do we call the following electronic circuits?
 i) A circuit that converts DC to AC
 ii) A circuit that convert DC to DC

10marks

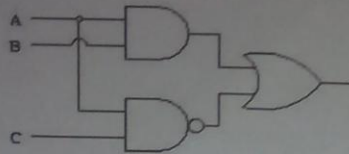18. (a) Write the Boolean expression for the circuit below.



- (b) Draw the logic circuit diagram for this expression $Y = (A + B) C$. Draw the truth table for each logic gate you used in the circuit diagram. **10marks**

19. (a) A pressurized tank must maintain a gas at 325psi. A pressure sensor is used to measure the condition of the controlled variable. As the gas cools, the pressure in the tank decreases. When it drops to 300 psi, a valve is opened, which allows steam to flow to a heat exchanger inside the tank. The additional steam heats the gas and causes the pressure to rise. **4marks**


- i) What is the controlled variable in this process?
 ii) What is the manipulated variable in this process?
 iii) What is the set point?
 iv) What is the measured variable?

- (b) What is the difference between a set point and a feedback signal?

10marks

- (c) List two examples of controlled variables for motion control applications and two examples for process control applications. **4marks**

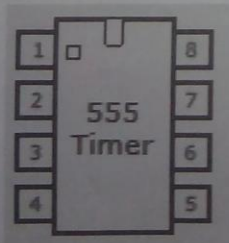20. a) Name the pins of 555 timer as they are respectively shown on the diagram below.




- b) Monostable 555 Timer is required to produce a time delay within a circuit. If a 10uF timing capacitor is used, calculate the value of the resistor required to produce a minimum output time delay of 500ms. **10marks**

**Section III. Answer any one (1) question of your choice
(Do not choose more than one question).**


15marks

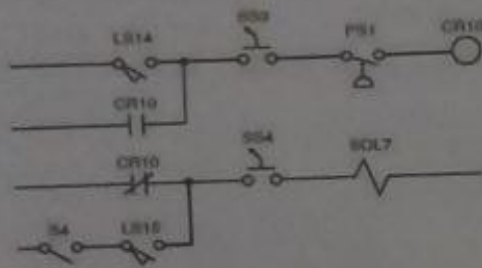21. Using the circuit shown in Figure below and starting inputs at address 10_{16} , outputs at address 50_{16} , and internals at address 100_{16} :
 (a) Assign the I/O addresses;
 (b) Draw the equivalent PLC ladder diagram.




15marks

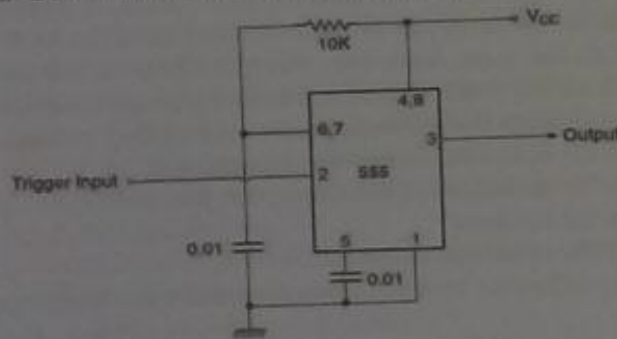22. Consider the Monostable multivibrator circuit in Fig. below. The trigger terminal (pin 2 of the IC) is driven by a symmetrical pulsed waveform of 10 kHz. Determine the frequency and duty cycle of the Output waveform.




15marks

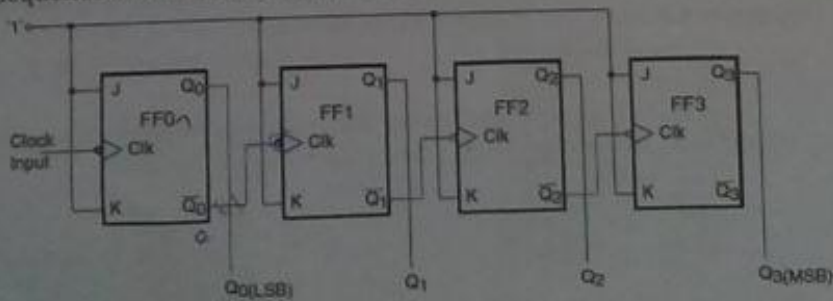23. Refer to the binary ripple counter arrangement of Fig. below. Write its count sequence if it is initially in the 0000 state. Also draw the timing waveforms.



15marks

SECTION I

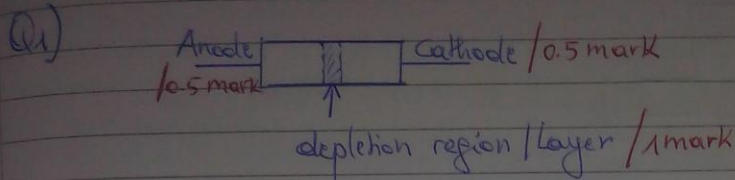

Q2)

$\begin{array}{r} 11011 \\ - 1001 \\ \hline 101 \\ - 100 \\ \hline 011 \\ - 000 \\ \hline 110 \\ - 100 \\ \hline 100 \\ - 100 \\ \hline 000 \end{array}$	$\begin{array}{r} 100 \\ 110.11_2 \\ \hline \end{array}$
--	--

1 mark

1 mark

1 mark


Q3) Four systems of arithmetic which are often used in digital circuits are:

- * Decimal number / 1 mark
- * Binary number / 1 mark
- * Octal number / 1 mark
- * Hexadecimal number / 1 mark

Q4) 3 types of multivibrators are:

- Monostable multivibrator (one shot) / 1 mark
- Bistable multivibrator / 1 mark
- Astable multivibrator (free running) / 1 mark

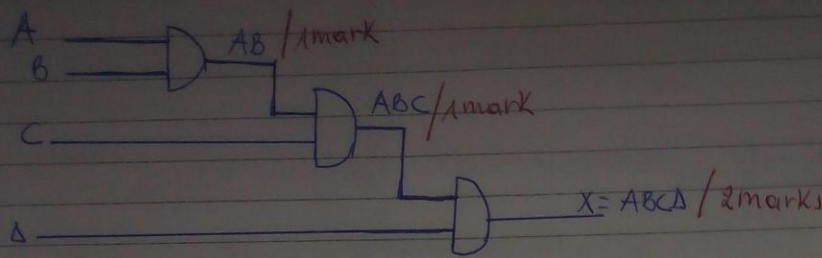Q5) The boolean expression for the figure below:



Do not write in this margin

Find the value when $A=B=C=D$ and $X=0$

$$X = ABCD$$

$$0 = 1 \cdot 1 \cdot 1 \cdot D$$

$$D = 0 \quad / 1 \text{ mark}$$

$$\text{or } [(AB)C]D = X \quad / 4 \text{ marks}$$

5 marks

Q6) The three important classes of devices used to build digital electronics systems are:

- Logic devices / 1 mark
- Memory devices / 1 mark
- Microprocessors / 1 mark

3 marks

Q7) The two categories of logic devices are:

- Programmable logic devices or sequential devices / 1 mark
- Fixed logic or combination devices / 1 mark

2 marks

Q8) Composition of a programmable logic array (PLA) devices are:

- Input / 0.5 mark
- Programmable AND array / 1 mark
- Programmable OR array / 1 mark
- Output / 0.5 mark

3 marks

Q9) - Ripple (Asynchronous/serial) counter / 2 marks
 - Synchronous or parallel counter / 2 marks

4 marks


Q10) The method used to load data onto and read from shifts registers are:

- sipo: Serial input parallel output / 1.5 marks
- siso: serial input ~~parallel~~ serial output / 1.5 marks
- piso: parallel input serial output / 1.5 marks
- pipso: parallel input parallel output / 1.5 marks

Q11) The number of Flip-flop required to construct:

- i) a MOD-10 ring counter is = 10 / 3 marks
- ii) a MOD-10 Johnson counter is = 5 / 3 marks

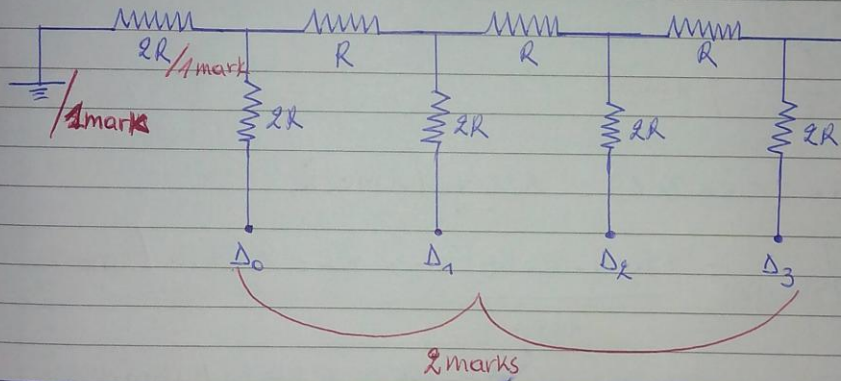Q12) Binary Ladder network used to convert digital to analogue is:



Q13) The types of Δ/A converters are:

- Multiplying system Δ/A converter / 1 mark
- Bipolar output Δ/A converter / 1 mark
- Companding Δ/A converter / 1 mark

Q14) A microprocessor is a programmable device that accepts binary data (from an input device processes, the data according to the instruction stored in the memory and provides result as output). In other words the microprocessor

0.5 mark

executes the program stored in the memory and transfers data to and from the outside world through input output path.
 1 mark
 1 mark

Do not write in this margin

2 marks

Q15) The two types of RAM are:

- SRAM (Static Random Access Memory) / 2 marks
- DRAM (Dynamic Random Access Memory) / 2 marks

4 marks

SECTION II

Q16) i) since field current remains the same

$$\phi_2 = \phi_1 \quad / 1 \text{ mark}$$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \quad / 1 \text{ mark}$$

$$E_{b1} = 200V - (0.5 \times 30A) = 185V \quad / 1 \text{ mark}$$

$$300 \text{ rpm} / 500 \text{ rpm} = \frac{(200V - 30R_f)}{185} \quad (\Rightarrow) R_f = 2.97 \Omega \quad / 1 \text{ mark}$$

$$\text{Addition resistance required} = 2.97 - 0.5 = 2.47 \Omega \quad / 1 \text{ mark}$$

ii) ~~$E_{b1} = \frac{V - I_a R_a}{s}$~~
 ~~$R_a = \frac{(500 - 200) \times 0.12}{476} = 0.0296 \Omega$~~

$$ii) \phi_2 = \frac{80 \phi_1}{100} = 0.8 \phi_1$$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{0.8 E_{b1}} \quad / 1 \text{ mark}$$

$$E_{b1} = V - I_a R_a$$

$$E_{b1} = 500 - (200 \times 0.12) = 476V \quad / 1 \text{ mark}$$

$$E_{b2} = V - I_{a2} \times R_a$$



$$E_{b2} = 500 - (100 \times 0.12)$$

$$E_{b2} = 500 - 12 = 488 \text{ V} / 1 \text{ mark}$$

then $N_2 = \frac{N_1 \times E_{b2}}{0.8 E_{b1}}$ ~~1 mark~~ $N_2 = \frac{250 \times 488}{0.8 \times 476} / 1 \text{ mark}$

$$N_2 = \frac{250 \times 488}{0.8 \times 476} = 320.38 \text{ rpm} / 1 \text{ mark}$$

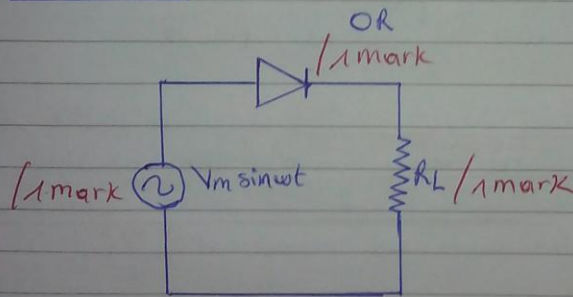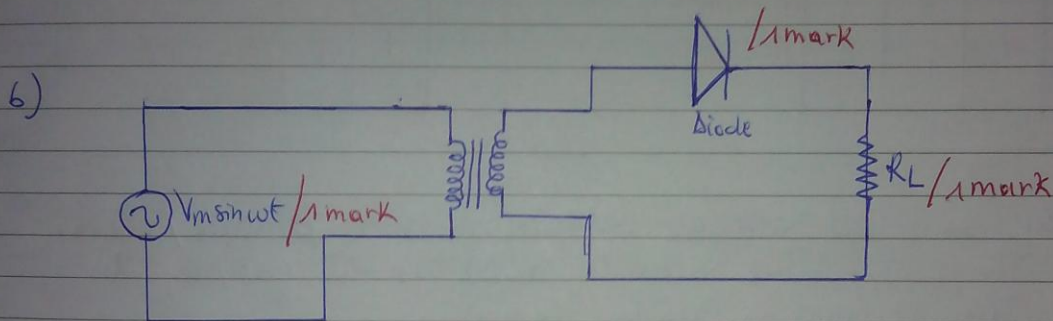Q17) a) Rectification is a process of converting from AC to DC by using rectifier (diode). / 2 marks



c) $V_{dc} = \frac{V_m}{\pi}$ / 3 marks where $V_m = V_{rms} \times \sqrt{2}$

where $V_m = V_{rms} \times \sqrt{2} - V_T$

OR


$V_{dc} = \frac{V_{rms} \times \sqrt{2} - V_T}{\pi}$ / 3 marks

d) Conversion from DC to AC the circuit is called inverter circuit / 1 mark

e) A conversion from AC to DC that circuit is called chopper circuit / 1 mark

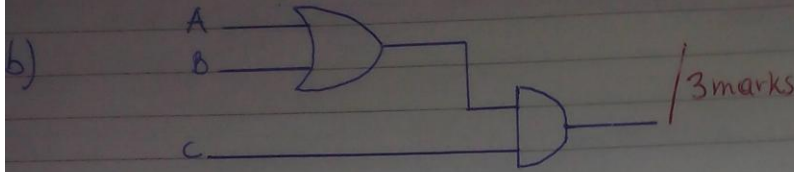Q18) a) The boolean expression of the circuit below is:

$$D = AB + \bar{A}C \quad / 3 \text{ marks}$$



OR Gate

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

/ 0.5 mark
/ 0.5 mark
/ 0.5 mark
/ 0.5 mark

AND gate

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

/ 0.5 mark
/ 0.5 mark
/ 0.5 mark
/ 0.5 mark

10 marks

- Q19) i) The controlled variable in this process is pressure / 1 mark
 ii) The manipulated variable ~~is~~ is the gas / 1 mark
 iii) The set point is 325 psi / 1 mark
 iv) The measured variable is 300 psi / 1 mark

b) The set point is prescribed input value applied to the loop that indicates the desired condition of the variable, while the feedback signal is the output of the measurement device, the feedback signal is the same as measured signal.

- c) Example of for motion control = - position / 1 mark
 - speed / 1 mark

Example for process control = - Flow rate / 1 mark
 - Temperature / 1 mark (only 2)
 - pressure / 1 mark

10 marks

- Q2c) a) pin 1: Ground / 1 mark
 pin 2: Trigger / 1 mark
 pin 3: out put / 1 mark
 pin 4: Reset / 1 mark
 pin 5: Control voltage / 1 mark
 pin 6: Threshold / 1 mark
 pin 7: Discharge / 1 mark
 pin 8: Supply (Vcc) / 1 mark

b) $\tau = 1.1 \cdot R_1 \cdot C_1$

$R_1 = \frac{\tau}{1.1 \cdot C_1} = \frac{0.5}{1.1 \times 10 \times 10^{-6}} = 45.5 \text{ k}\Omega$ / 1 mark

SECTION III


Q2d)

a) The I/O addresses

Module type	I/O addresses			Description
	Bank	Group	Terminal	
Input	0	1	0	LS14
	0	1	1	SS3
	0	1	2	PS1
	0	1	3	S4
	0	1	4	LS15
	0	1	5	SS4
	0	1	6	-
	0	1	7	-
output	0	5	0	SOL 7
Internal	1	0	0	CR10

/1 mark /1 mark /1 mark /1 mark /1 mark

b) The equivalent PLC ladder diagram

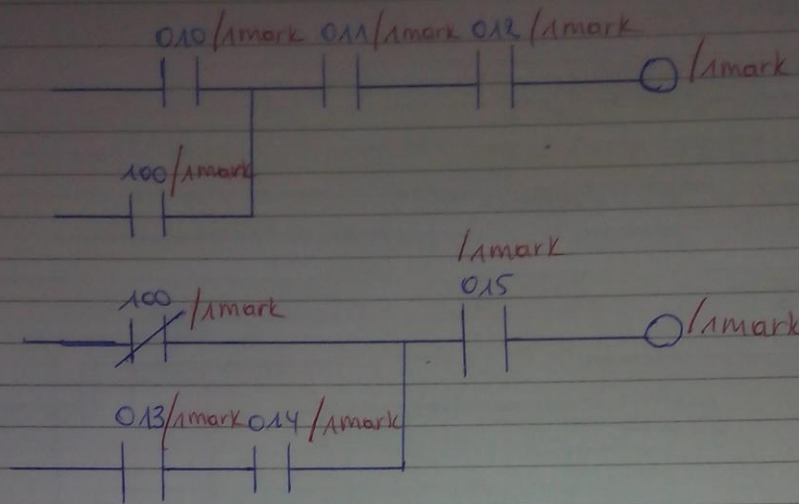

Do not write in this margin

15 marks

Q22) The frequency of the trigger wave form = 10KHz / 1mark

$$T_{\text{trigger}} = \frac{1}{f_{\text{trigger}}} = \frac{1}{10 \times 10^3} = 10^{-4} \text{ sec} = 100 \mu\text{s} / 1 \text{ mark}$$

$$T_{\text{ON}} = 1.1 R-C = 1.1 \times 10^4 \times 10^{-8} = 1.1 \times 10^{-4} \text{ sec} = 110 \mu\text{s} / 1 \text{ mark}$$

Because we have symmetrical pulse

$$T_H = T_L / 1 \text{ mark}$$

$$T_H + T_L = T_{\text{trigger}}$$

$$T_L = \frac{T_{\text{trigger}}}{2} = \frac{10^{-4}}{2} = 0.5 \times 10^{-4} \text{ sec} = 50 \mu\text{s} / 1 \text{ mark}$$

$$f_{\text{out}} = \frac{f_{\text{trigger}}}{2} = \frac{10 \text{ kHz}}{2} = 5 \times 10^3 \text{ Hz} = 5 \text{ kHz} / 1 \text{ mark}$$

$$T_{\text{out}} = \frac{1}{f_{\text{out}}} = \frac{1}{5 \times 10^3} = 2 \times 10^{-4} \text{ sec} = 200 \mu\text{s} / 2 \text{ marks}$$

$$d = \frac{T_{\text{ON}}}{T_{\text{out}}} = \frac{1.1 \times 10^{-4}}{2 \times 10^{-4}} = 0.55 \text{ or } d = 55\% / 2 \text{ marks}$$

15 marks

~~Comments: The ~~twenty~~ see The ~~question~~ number twenty-bit~~


on this question the capacitor given doesn't have a unit. Reason why any student who will attempt it using formulas only will get maximum of marks.

Q23)


pulses	Q ₀	Q ₁	Q ₂	Q ₃	
0	0	0	0	0	
1	1	1	1	1	/0.5 mark
2	0	1	1	1	/0.5 mark
3	1	0	1	1	/0.5 mark
4	0	0	1	1	/0.5 mark
5	1	1	0	1	/0.5 mark
6	0	1	0	1	/0.5 mark
7	1	0	0	1	/0.5 mark
8	0	0	0	1	/0.5 mark
9	1	1	1	0	/0.5 mark
10	0	1	1	0	/0.5 mark
11	1	0	1	0	/0.5 mark
12	0	0	1	0	/0.5 mark
13	1	1	0	0	/0.5 mark
14	0	1	0	0	/0.5 mark
15	1	0	0	0	/0.5 mark
16	0	0	0	0	/0.5 mark

The timing waveforms are shown below. Thus we have a four bit counter that counts in the reverse sequence, beginning with the maximum count. This is a down counter.


Do not write in this margin

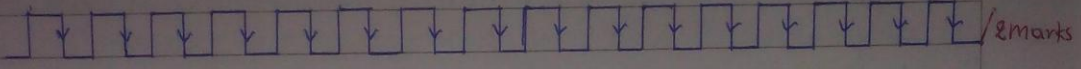


/2 marks

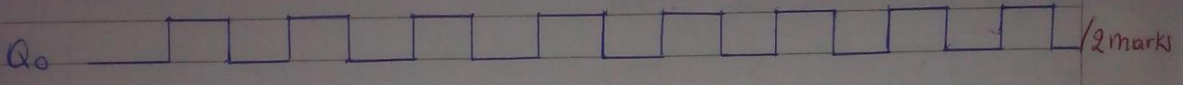


/2 marks

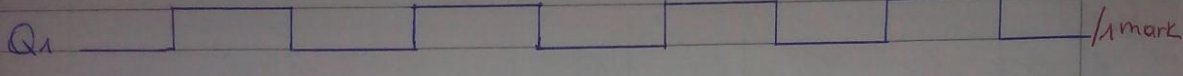

/1 mark

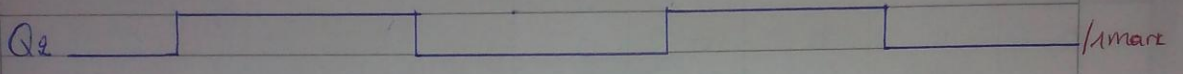

/1 mark

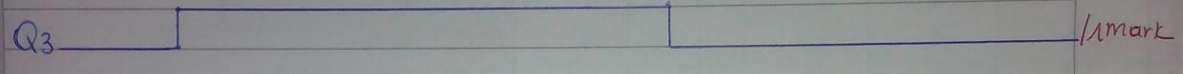

/1 mark

15 marks