

**CEL & ETL - Analog and
Digital Systems**

T005

Friday, 31/10/2014

01:30 - 04:30 PM

WORKFORCE DEVELOPMENT AUTHORITY



P.O. BOX 2707 Kigali, Rwanda Tel: (+250) 255113365

**ADVANCED LEVEL NATIONAL EXAMINATIONS, 2014
TECHNICAL AND PROFESSIONAL TRADES**

EXAM TITLE: Analog and Digital Systems

OPTIONS: - Computer Electronics (CEL)

- Electronics and Telecommunication (ETL)

DURATION: 3hours


INSTRUCTIONS:

The paper consists of **three (3) Sections :**

Section I: Fourteen (14) questions, all Compulsory.	55marks
Section II: Five (5) questions, Choose any Three (3).	30marks
Section III: Three (3) questions, Choose any One (1).	15marks

SECTION I. FOURTEEN (14) COMPULSORY QUESTIONS.

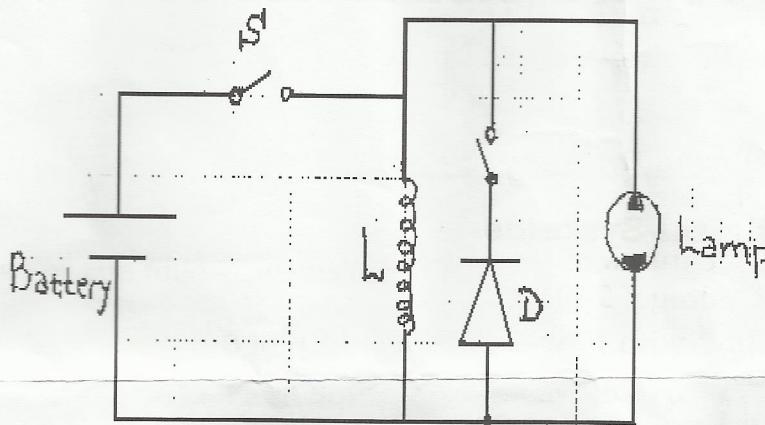
- Q1.** Find the canonical form of the following Boolean expression : **3marks**
 $F(A,B,C) = AB + BC$.
- Q2.** Design a D flip-flop from a J-K flip-flop. **2marks**
- Q3.** What should be done to unused inputs on TTL gates? **5marks**
- Q4.** Which functions a GTO gate drive circuit has to fulfill? **4marks**
- Q5.** Identify two (2) different methods to represent basic logic functions. **2marks**
- Q6.** Explain the functioning of the following circuit by turning ON and switch off quickly that circuit : **4marks**



- a) Without diode; b) With diode mounted. **4marks**
- Q7.** Identify the component of a typical transducer measurement system bloc (output digital). **5marks**
- Q8.** Identify the components of the 555 timer. **5marks**
- Q9.** Identify any five (5) methods of thyristor turn on. **5marks**
- Q10.** Specify two (2) different methods of voltage control inverters. **2marks**
- Q11.** Describe the function of freewheeling diode in a controlled rectifier circuit. **3marks**
- Q12.** Identify any five (5) characteristics of an amplifier that are modified by negative feedback. **5marks**
- Q13.** Simplify the following expression using Boolean algebra technique
 $Z = AB + A(B + C) + B(B + C)$. **5marks**
- Q14.** Identify five (5) applications of AC voltage controllers. **5marks**

SECTION II. ATTEMPT ANY THREE (3) QUESTIONS.

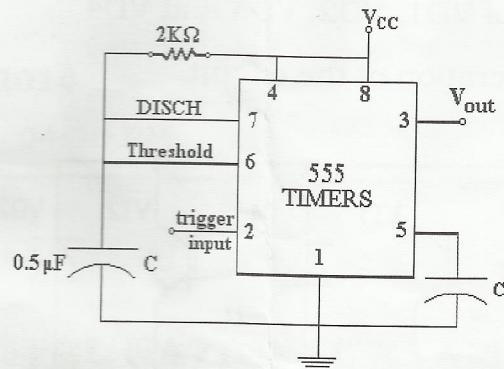- 15. a)** Find the period (in msec) of the output pulse in the circuit shown below and give a name at this circuit. **5marks**




- b)** Show how a full adder may be implemented by using two half adders. **5marks**

- 16.** Describe the basic operation of a single-slope analog to digital converter. **10marks**

- 17.** Identify the logic families according to the technology they are built with and specify which family is widely used. **10marks**

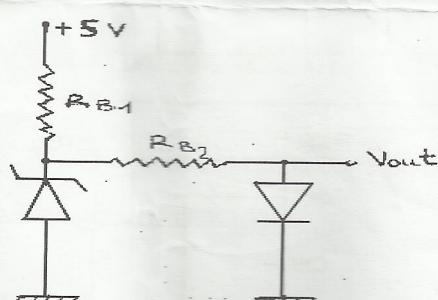- 18.** In the following circuit, the specifications of zener diode at 25°C are: **(1°)** bias current: 10mA; **(2°)** output voltage: 2495mV

The diode is forward biased at 2mA with forward voltage drop of 0.55V;




Determine R_{B_1} and R_{B_2} and select both values of resistors from the list of 1% decade values. **10marks**

- 19. a)** For the circuit below, determine the function performed; the role of S₁, R_b, C_b and S₂.

- b)** Determine different modes of operation of that circuit.

10marks

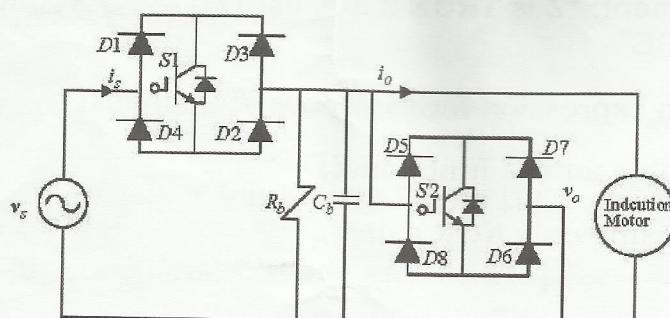


SECTION III. ATTEMPT ANY ONE (1) QUESTION.

20. Consider the circuit below and answer to the following questions :

- Determine the type of circuit and its characteristics
- What is the function of VD1, VD2, VD3 and VD4
- Explain briefly the operation of the circuit.


15marks

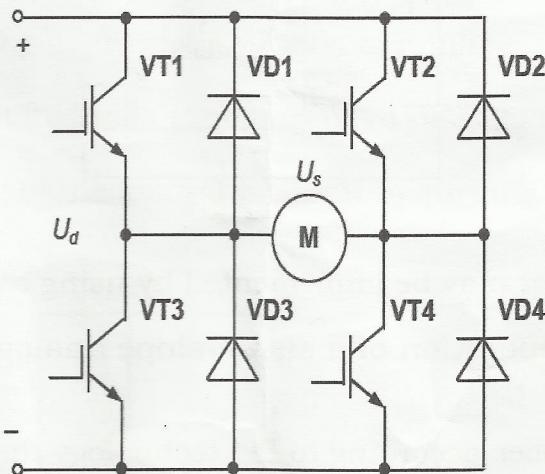

21. For the following circuit,

- Identify the main functional parts.
- Study the behavior.

15marks

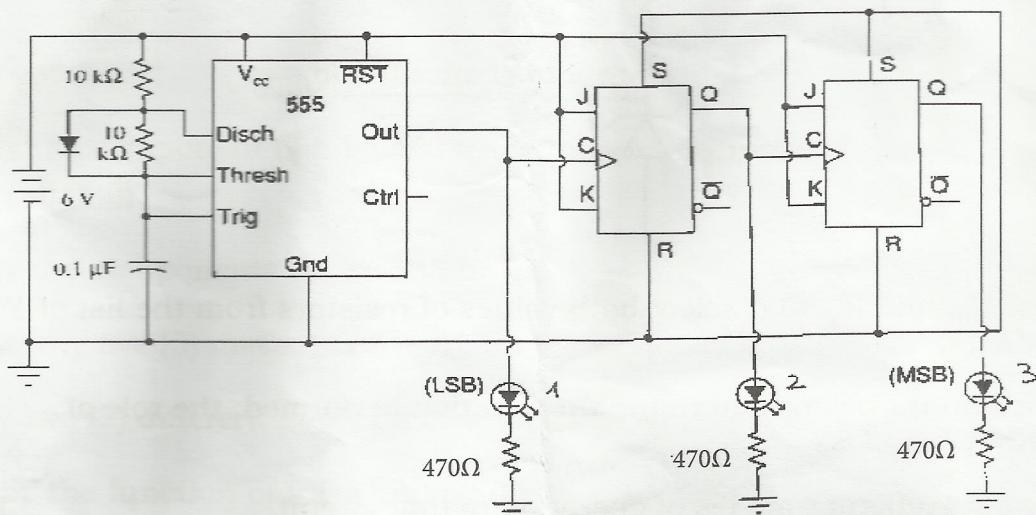

22. Consider the statement: "Z is TRUE if at least two of W, X and Y are TRUE", otherwise Z is FALSE".

- Write a Boolean expression for the above statement.
- Write a truth table for the function Z;
- Implements Z using only NOR gates.

15marks

SECTION I.

Do not
write in
this margin

01. $F(A, B, C) = AB + BC$

canonical form:


$$AB + BC = AB(C + \bar{C}) + (A + \bar{A})BC \quad 1\text{mark}$$

$$= ABC + A\bar{B}C + ABC + \bar{A}\bar{B}C \quad 1\text{mark}$$

$$F(A, B, C) = ABC + A\bar{B}C + \bar{A}\bar{B}C \quad 1\text{mark}$$

3marks.

02. D Flip-Flop from a J-K Flip-Flop.

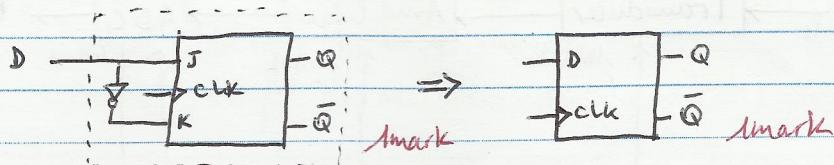

03. • Unused AND & NAND inputs should be tied to Vcc through a 1kΩ resistor ^{1mark} _{1mark}

• Unused OR & NOR inputs should be grounded. ^{1mark} _{1mark} ^{1mark} _{1mark} ^{5marks}

04. GTO gate drive circuit has to fulfill the following functions:

- 1) Turn on the GTO ^{1mark}
- 2) Turn off the GTO ^{1mark}
- 3) Maintain conduction ^{1mark}
- 4) Reinforce the blocking ^{1mark}

4marks

05. Methods to represent basic logic functions are:

- Truth table ^{1mark}
- Boolean algebra expression ^{1mark}
- Traditional graphic logic symbols ^{1mark}
- Timing diagrams ^{1mark}
- Logical statement ^{1mark}

choose only two

2mark

06. a) without diode :

when the switch is opened after it was closed,
the lamp will flash from the effect of inductive kick back


1mark

b) With diode mounted

Quickly close and open the circuit, this time the lamp will not
flash, because the diode eliminates the kick back effect
creating a short circuit for the lamp.

4marks.

07.

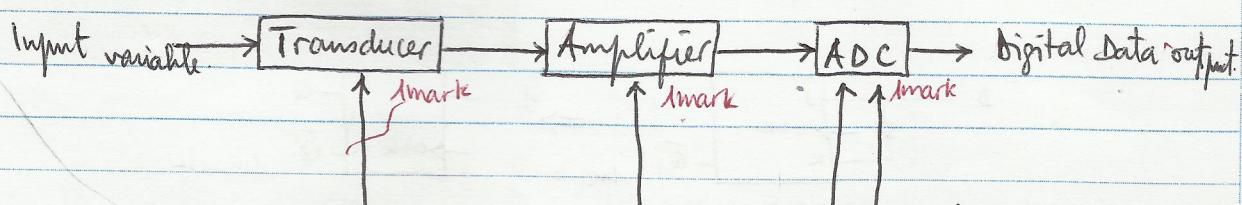

ADC: Analog to Digital converter.

- OR
- 1) Transducer 1mark
 - 2) Amplifier 1mark
 - 3) ADC 1mark
 - 4) Power Supply 1mark
 - 5) Bias circuit or excitation circuit 1mark
 - 6) Digital control 1mark
- Choose only five

5marks.


08.

Components of 555 timer

- Resistors (3) 1mark
- Comparators (2) 1mark
- Transistors (2) 1mark
- Flip flop (1) 1mark
- Output drive (1) 1mark

5marks.

OR

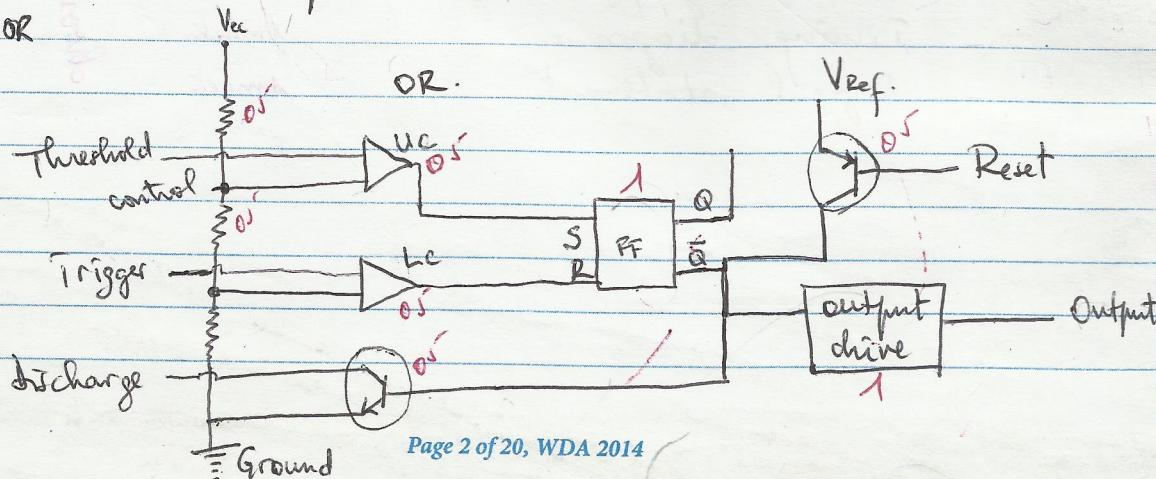

09. Thyristor turn on methods :

- Forward voltage triggering 1mark
- Gate triggering 1mark
- Temperature / thermal triggering 1mark
- light triggering 1mark
- $\frac{dv}{dt}$ triggering 1mark

5marks

10. Methods of voltage control inverters :

- Control DC input voltage 1mark
- Control AC output voltage 1mark
- Control voltage within inverter 1mark
- Control using PWM (pulse width modulate) 1mark

Choose only
two.

2marks

11. The function of freewheeling diode :

- It prevents the output voltage from becoming negative 1mark
- The load current is transferred from the main thyristors to the freewheeling diode, thereby allowing all of its thyristors to regain the main blocking states. 1mark

3marks

12. Characteristics of an amplifier modified by negative feedback :

- Sensitivity of transfer characteristics 1mark
- Non linear distortion 1mark
- Frequency response (Harmonic) 1mark
- Noise 1mark
- Bandwidth. 1mark
- Input & output impedance of amplifier. 1mark
- Gain of voltage 1mark

Choose only five

5marks

$$Z = AB + A(B+C) + B(B+C)$$

$$= AB + AB + AC + BB + BC \quad 1mark \quad BB = B$$

$$= AB + AC + B + BC \quad 1mark$$

$$= AB + AC + B(1+C) \quad 1mark \quad \therefore B(B+C) = B \cdot 1 = B$$

$$= B(A+1) + AC \quad 1mark \quad \therefore A+1 = 1$$

$$\therefore Z = B + AC \quad 1mark$$

5marks

(Show) $2f_130m + n_{13} \text{ for } 13f = 2f_{13}$

(Show) n_{13}

(Show)

14. Applications of voltage controllers :

- Lighting (dimmers) 1mark
- Induction motor 1mark
- Inverters 1mark
- Automatic voltage Regulator (VAR) compensation 1mark
- Aircraft 1mark

5marks.

SECTION II.

15. a) The name of given circuit is : Monostable multivibrator 2marks

- The period of output pulse :

$$T = 1.1RC = 1.1 \times 2 \times 10^3 \times 0.5 \times 10^{-6}$$

1mark

$$= 1.1 \times 10^3 \text{ sec. } 1\text{mark}$$

$$= 1.1 \text{ msec. } 1\text{mark}$$


b) Construction of full adder from two Half adders :

- Half adder : Truth table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Sum (S) = $A \oplus B$ 1mark
 Carry (C) = AB


logical circuit of Half adder

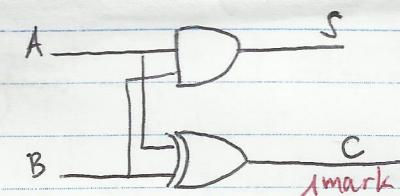

- Full adder is a combination of two Half adders :

A	B	C_{in}	S_0	C_0
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

logical circuit of full adder

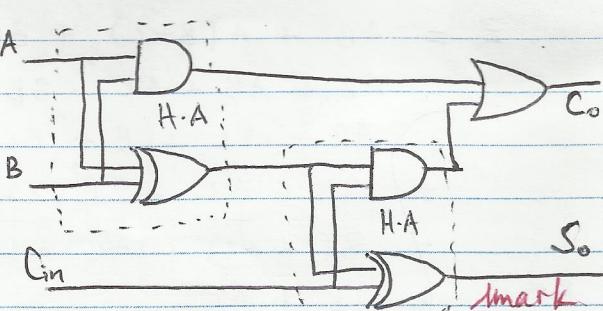

Sum (S_0) = $A \oplus B \oplus C_{in}$ 1mark

Carry (C_0) = $AB + C_{in}(A \oplus B)$ 1mark

Note : The final circuit merits all marks. 10marks

16. Single-slope Analog to Digital Converter:

A ramp generator is used to enable a counter through the comparator. When the ramp voltage equals to the input voltage, the counter is latched and then reset. The counter reading is proportional to the input voltage since the ramp is changing at a constant voltage per second rate.

10marks

① 17. The logic families are:

- | | |
|-----------------------|--|
| Bipolar logic family | <ul style="list-style-type: none"> - RCTL: Resistor capacitor Transistor logic 1mark - DCTL: Direct coupled Transistor logic 1mark - RTL: Resistor Transistor logic 1mark - DTL: Diode Transistor logic 1mark - HTL: High Threshold logic 1mark - TTL: Transistor Transistor logic 1mark - I²L: Integrated Injection logic (merged Transistor logic) 1mark - STTL: Schottky Transistor Transistor logic 1mark - ECL: Emitter Coupled logic 1mark |
| Unipolar logic family | <ul style="list-style-type: none"> - MOS (n-MOS & p-MOS): Metal Oxide Semiconductor 1mark - CMOS: Complement Metal Oxide Semiconductor 1mark |
- The widely used family is MOS. 2marks.

Choose only eight

10marks

18. We determine I through R_{B1}:

$$I = I_Z + I_D = 10 + 2 = 12 \text{mA} \quad \text{1mark}$$

$$R_{B1} = \frac{E - V_Z}{I} = \frac{5 - 2.495}{0.012} = 208 \Omega \quad \text{1mark} \quad \text{1mark}$$

$$R_{B2} = \frac{V_Z - V_D}{I_D} = \frac{2.495 - 0.55}{0.002} = 972.5 \Omega \quad \text{1mark} \quad \text{1mark}$$

In list of 1% decade values:

$$R_{B1} = 208 + (208 \times 1\%) = 210 \Omega \quad \text{1mark}$$

$$R_{B2} = 972.5 + (972.5 \times 1\%) = 982 \Omega \quad \text{1mark}$$

10marks

19. a) * The function performed is to control (run) the motor in two directions (forward & reverse). 1mark

* Role of:

S₁: Switching device used in forward direction 1mark

S₂: Switch which controls the reverse motion 1mark

R_b: (Resistor used for) regulation of voltage or protection 1mark

C_b: Shunt filter 1mark against overcurrent 1mark

Do not write in this margin

- b) Modes of operation: - Forward operation 2marks
- Reverse operation 2marks

10marks.

SECTION III .

20. a) The type of the circuit is :- H-bridge

- Inverter 2marks

- DC motor direction control

Characteristics: - 4 switches : V_{T1}, V_{T2}, V_{T3}, V_{T4}. 1mark

- Two diagonal switches work simultaneously i.e. V_{T1} + V_{T4} and V_{T2} + V_{T3}. 1mark

- The source power is DC signal 1mark

- The output power is AC signal (square wave) 1mark

- It has 4 protective diodes (V_{D1}, V_{D2}, V_{D3}, V_{D4}) 1mark

b) The function of V_{D1}, V_{D2}, V_{D3}, V_{D4} : is for protection of switches against back voltage 2marks

c) According to shown polarities, when the gate signals are applied correctly, V_{T1} & V_{T4} will run the motor M in forward direction. 1mark In this case V_{T2} & V_{T3} are off. 1mark

After V_{T1} & V_{T4} are switched OFF by removing the gate signal, then V_{T2} & V_{T3} will be switched ON by triggering them. This means that the motor will run in reverse direction. 1mark

OR

Forward motion (direction) : + V_{T1} → M → V_{T4} → - 1mark 1mark 05 marks

Reverse motion : + V_{T2} → M → V_{T3} → - 1mark 1mark 1mark 05 marks

15marks

Q1. a) Main functional parts:

- clock pulse generator with 555 IC 1mark
- Modulus 4 Counter with J-K FF 1mark
- Display unit : LED 1mark
- Power Supply : 6V 1mark

b) Circuit behavior:

- The 555 timer (IC) powered generates pulses. 1mark
- . The pulses are applied on the 1st J-K FF which is connected as a ^{divider 1}_{1mark}, then it will change state when it receives a pulse. The output of 1st FF is used as clock pulse for the second Flip Flop which is also connected as ^{divider 2}_{1mark}. It will change state also when it receives clock pulse from JK Flip Flop 1.

The LED₂ & LED₃ show the state of FFs. 1mark

The LED₁ shows frequency of pulse generator. 1mark

The circuit is an asynchronous counter. 1mark
(ripple)

15marks


Q2. a) Boolean expression: $\bar{W}XY + W\bar{X}Y + WX\bar{Y} + WXY$

_{1mark} _{1mark} _{1mark} _{1mark}

b) Truth table:

w	x	y	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

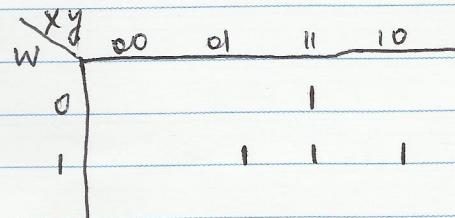c) Simplify Boolean expression (Using K-map)




$$Z = XY + WY + WX. \quad 1mark$$

Implementation using NOR gates.

$$Z = \overline{\overline{Z}} = \overline{\overline{xy} + wx + \overline{w}x} \quad 1\text{mark}$$

$$= \overline{(\bar{x} + \bar{y})(\bar{w} + \bar{y})(\bar{w} + \bar{x})} \quad \cancel{1\text{mark}}$$
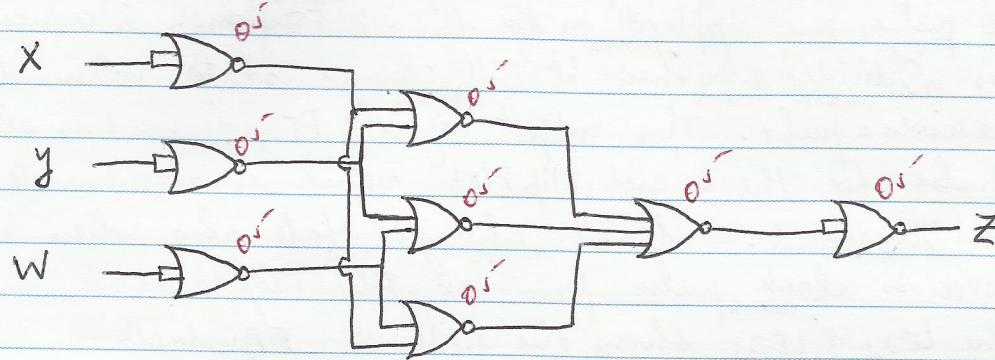
$$= \overline{\bar{x} + \bar{y}} + \overline{\bar{w} + \bar{y}} + \overline{\bar{w} + \bar{x}} \quad \cancel{1\text{mark}}$$



15 marks